



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY
jou kennisvennoot • your knowledge partner

E344 Assignment 6

Frank Harraway
22623280

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

September 30, 2021



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY
jou kennisvennoot • your knowledge partner

Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present is as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.


I also understand that direct translations are plagiarism.

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

22623280	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
F. Harraway	September 30, 2021
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

Contents

Declaration	i
List of Figures	iii
List of Tables	iv
Nomenclature	v
1. Battery 0-5V	1
1.1. Literature	1
1.2. Design	1
1.3. Results	2
2. Bidirectional current measurement	3
2.1. Overview	3
2.2. Literature	3
2.3. Design	3
2.4. Results	4
Bibliography	5
A. GitHub Activity Heatmap	6
B. Calculations	7

List of Figures

1.1. Battery Voltage Conditioning Circuit	2
---	---

List of Tables

Nomenclature

Variables and functions

V_O	The output voltage of the TSC213.
V_{swing}	The output swing of the TSC213.
V_{ref}	The reference voltage of the TSC213.
I_{range}	The current range that the TSC213 is designed for.
R_{shunt}	The resistor value that the TSC213 will measure a differential voltage across.
C	Capacitance used in lowpass circuit.

Acronyms and abbreviations

A	Ampere
μ	micro-
m	mili-
k	kilo-
V	Volts
NMOS	N-channel metal-oxide semiconductor
PMOS	P-channel metal-oxide semiconductor
op amp	Operational Amplifier
LED	Light emitting diode
Ω	Ohms- a measure of resistance
Hz	Hertz- a measure of frequency
F	Fare- a measuremnt of Capacitance

Chapter 1

Battery 0-5V

1.1. Literature

1.2. Design

In this design the battery voltage will go through a signal conditioning process to make it readable from the perspective of an ADC. The ADC we are going to use requires a voltage between 0 and 5V. The battery voltage will vary between 6V and 7.2V if the complete system is working as designed. For the purpose of the design an additional 0.3V will be extended on to either side of the boundaries (5.7V to 7.5V). Using Op Amps the battery voltage will be designed to vary linearly with an output swing of 3.5V. This 3.5V will be equally spaced from the 0 and 5V boundaries of the ADC (0.75V to 4.25V), the output swing is chosen to be less than 5V in order to prevent possible damage to the ADC in the case that the reconditioned battery voltage exceeds 5V.

The immediate problems faced is that the lowest battery voltage is not 0V but rather 5.7V. This means that the battery voltage will require a shift in order for the design requirements above to be met. This is achieved with an inverting op amp with a reference voltage. The voltages as they are will have to be divided down in order not to breach the differential voltage limits of the MCP op amps that are being used ($|V_{ss} - V_{dd}|$ [1]). This can be seen in the voltage following section of figure 1.1. A voltage follower is used to prevent the negative feedback of the inverting op amp from interfering with the divided battery voltage. The output of the non inverting amplifier is significantly smaller than the requirements. Therefore a non inverting amplifier is then used to amplify this output to required levels. To calculate suitable values I worked backwards from the output to the input.

$$V_{out-invert} = 2 \times V_{invert-ref} + (-1) \times \left(\frac{R_{F1}}{R_{in1}}\right) \times V_{invert-in} \quad (1.1)$$

$$V_{noninvert-out} = \left(1 + \frac{R_{F2}}{R_x}\right) \times V_{out-invert} \quad (1.2)$$

The non inverting amplifier is chosen to have a gain of 15. This means that to achieve the output range "0.75V to 4.25V" the non inverting amplifier requires 15 times less than the output "50mV to 283.3mV". Due to using an inverting amplifier the point at which the

inverting output is 283.3mV the battery voltage will be 5.7V and when the inverting output is 50mV the battery voltage will be 7.5V. Using eq.1.1 and solving simultaneously for $V_{invert-in}$ ($V_{invert-in} = V_{bat} \times \frac{R_2}{R_2+R_1}$). The inverting amplifier is designed to have unity gain as it only serves the purpose of shifting the battery voltage down. The resistor values are then found to be , $R_1=180k\Omega$ and $R_2=27k\Omega$. Detailed calculations can be found at appendix B. $V_{invert-ref}$ is calculated to be 511mV and is implemented by dividing the 5V regulator voltage with R_3 and R_4 (refer to figure 1.1).

To achieve a gain of 15 for the non inverting amplifier ($1+\frac{R_{F2}}{R_x}$ from eq.1.2) must be equal to 15. R_{F2} is chosen to be 150k Ω and R_x is calculated to be 10.71k Ω . Two lab 22k Ω resistors in parallel are used to implement R_x (refer to 1.1).

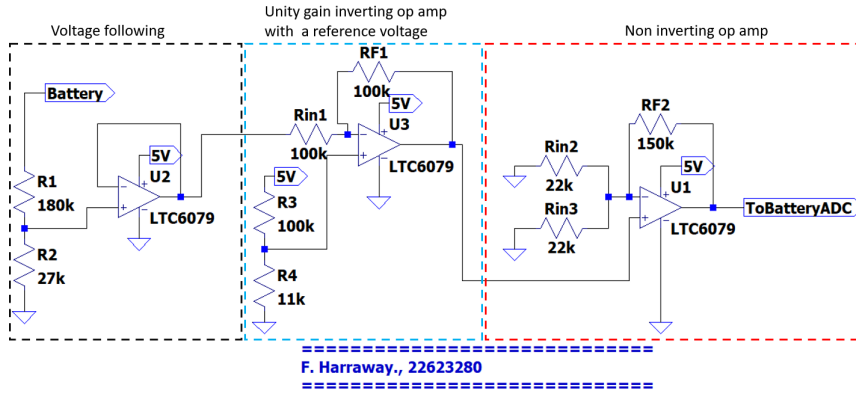


Figure 1.1: Battery Voltage Conditioning Circuit

1.3. Results

Chapter 2

Bidirectional current measurement

2.1. Overview

2.2. Literature

2.3. Design


2.4. Results

Bibliography

- [1] Microchip Technology, “Mcp6241/1r/1u/2/4,” 2008. [Online]. Available: https://learn.sun.ac.za/pluginfile.php/2893569/mod_resource/content/0/MCP6241.pdf

Appendix A

GitHub Activity Heatmap

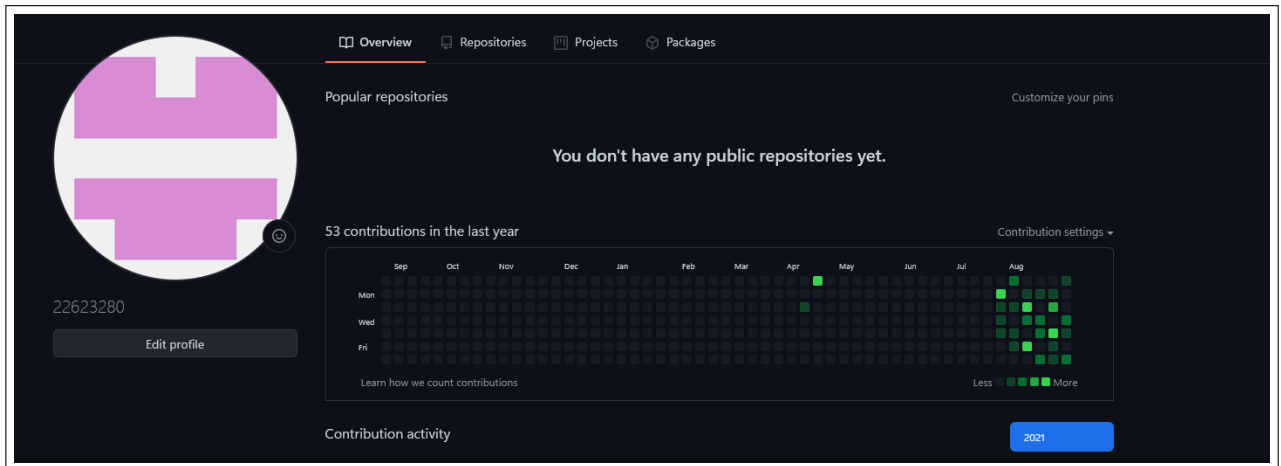

Appendix B

Calculations

$$V_{out-invert} = 2 \times V_{invert-ref} + (-1) \times \left(\frac{R_{F1}}{R_{in1}}\right) \times V_{invert-in} \quad (B.1)$$

$$V_{invert-in} = \frac{R_2}{R_2 + R_1} \times V_{bat} \quad (B.2)$$

$$V_{noninvert-out} = \left(1 + \frac{R_{F2}}{R_x}\right) \times V_{out-invert} \quad (B.3)$$

Using eq.B.2 and B.1 the equation below is setup.

$$\frac{R_2}{R_1 + R_2} = \frac{2 \times V_{invert-ref} - 283.3mV}{5.7} = \frac{2 \times V_{invert-ref} - 50mV}{7.5}$$

$V_{invert-ref} = 511mV$ R_1 chosen to be 180k and $R_2 = 26.8k\Omega$ (lab resistor is 27k Ω)